




2nd Semester, 2023-2024

MCT232: Electronics for Instrumentation


Sheet 1

Problem 1: Assume ideal opamps determine the voltage transfer gain $T = v_O/v_S$ and input resistance R_{in} for each of the configurations by inspection. (Resistances are in $k\Omega$).

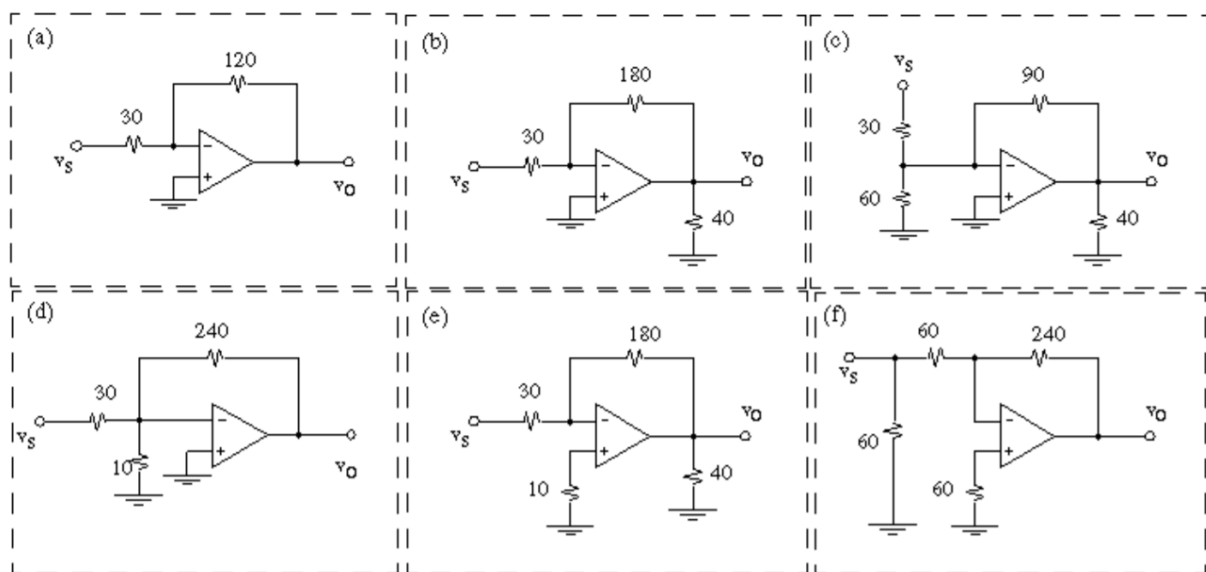


Problem 2: (a) Using resistances no larger than 1.0 $M\Omega$ design an amplifier with gain -20 V/V and the largest possible R_{in} , using the inverting configuration. Assume ideal opamp.



(b) What is the input resistance?

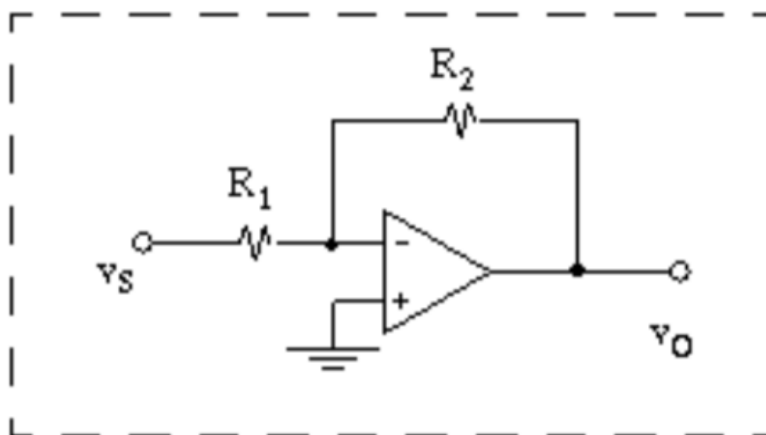



Problem 3: Find (a) transfer function $T = v_O/v_S$ and (b) input resistance R_{in} . (Resistances are in $k\Omega$)

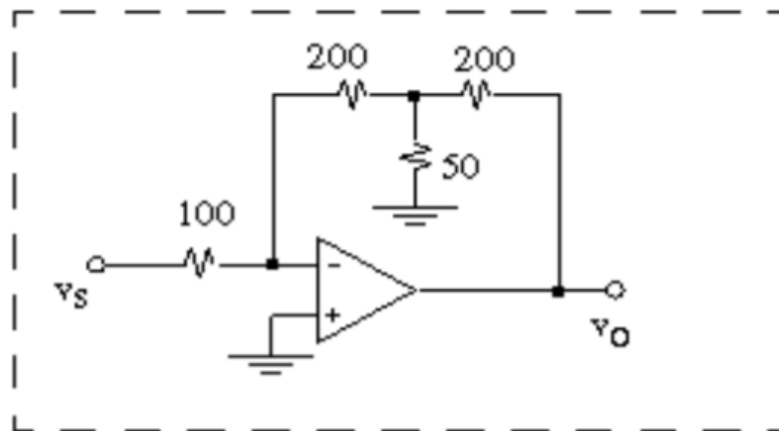


Problem 4: Find (a) transfer gain $T = v_O/v_S$ and (b) input resistance R_{in}

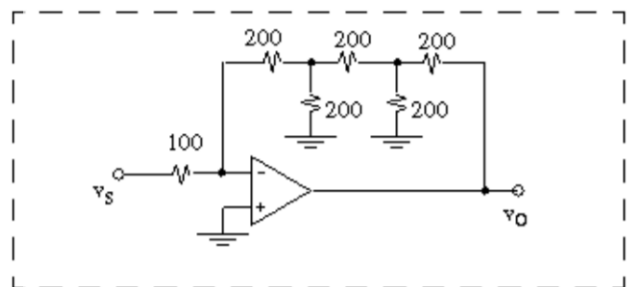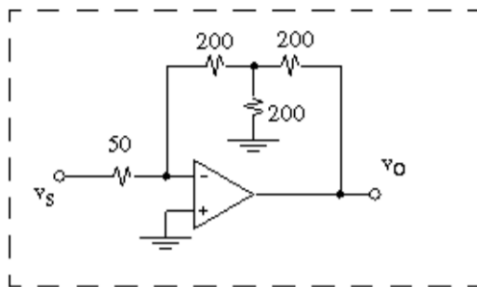

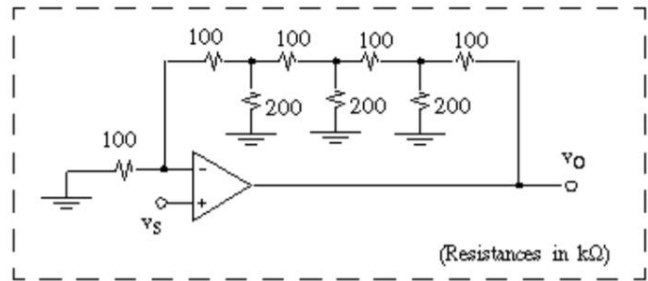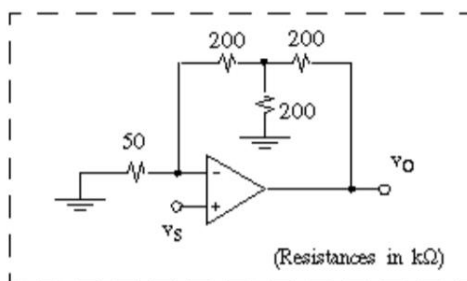
Problem 5: Find transfer gain $T = v_O/v_S$, input resistance



Problem 6: (a) Using the inverting configuration with single-tee feedback (as shown) and resistances no larger than 600 k Ω , design an amplifier with gain -12 V/V and the largest possible R_{in} . Assume ideal opamp. (b) What is the R_{in} ?

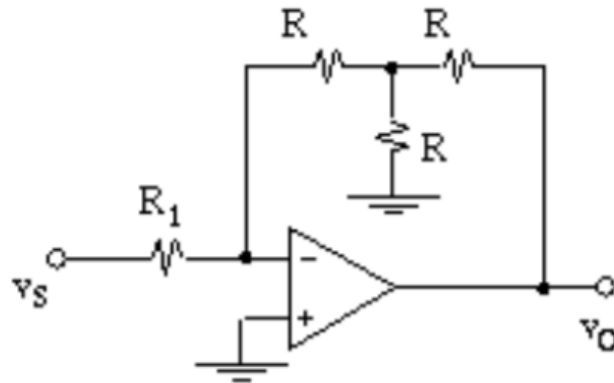

Problem 7: Find the transfer function $T = v_O/v_S$

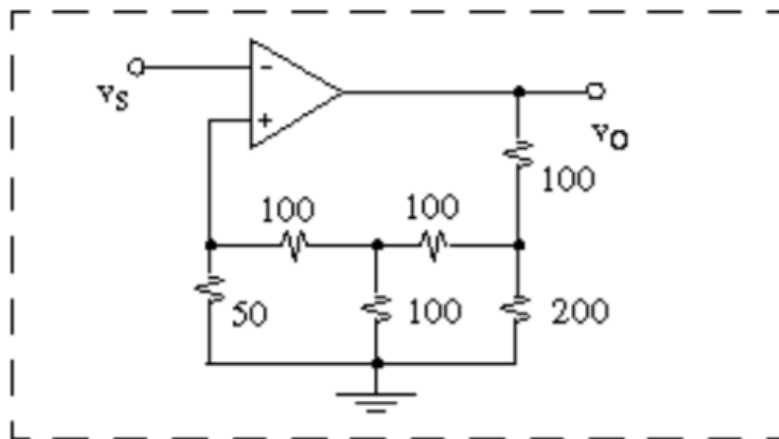

Problem 8: Determine input resistance R_{in} and transfer gain v_O/v_S for the circuit shown, assuming that (a) $R_f = \infty$ (b) $R_f = 100\text{k}\Omega$

